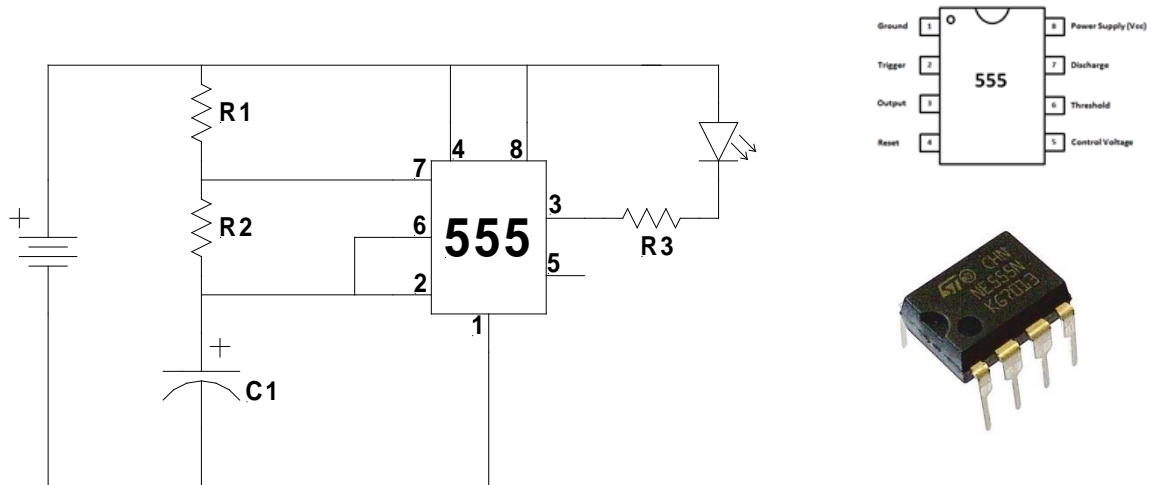


Breadboard Lab #9

“A blinking light using a 555 Integrated Circuit”

- 1) Breadboard the following schematic diagram. Set the Power Supply to 9 volts.



R1: 1K ohm
R2: 10K ohm

R3: 330 ohm
C1: 100uf

- 1) When you connect the circuit to power, the LED will blink. The blink occurs when the voltage at pin #3 alternates between 0 volts (low) and 9 volts (high). Changing the values of R1, R2 and C1 changes the frequency at which the LED blinks. Replace C1 with a 10uf capacitor. Replace R1 with a 100k resistor. Carefully watch what happens to the blinking. Use the [Electronic Components PowerPoint presentation](#) from class to help.

- 2) Answer the following questions

- a) The output of this circuit (pin #3) produces a _____ and _____ voltage alternately that cause the LED to flash.
- b) The frequency at which the LED blinks is controlled by _____, _____ and _____.
- c) The larger the values of the resistors and capacitor, the _____ the frequency of pulses.
- d) What happens if the value of R1 is bigger than R2?